

Formulari Electrotècnia M09 UF2

Corrent altern

$$V(t) = V_{\max} \cdot \sin(\omega \cdot t + \phi) \quad (V) \quad (\text{Utilitzar la calculadora en radians (R)})$$

$$\omega = 2 \cdot \pi \cdot f \quad (\text{rad/s}) \quad T = 1/f \quad (s) \quad f \quad (\text{Hz})$$

$$V_{\text{ef}} = V_{\max} / \sqrt{2} \quad (V)$$

Impedàncies i llei d'ohm

$$X_L = 2 \cdot \pi \cdot f \cdot L \quad X_C = \frac{1}{2 \cdot \pi \cdot f \cdot C} \quad Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (\Omega)$$

$$V_R = R \cdot I_R \quad V_L = X_L \cdot I_L \quad V_C = X_C \cdot I_C \quad V_T = I_T \cdot Z \quad (V)$$

$$I_T = V_T / Z \quad (A)$$

Potències


$$P = V_R \cdot I_R = R \cdot I_R^2 = V_R^2 / R \quad (W)$$

$$Q_L = V_L \cdot I_L = X_L \cdot I_L^2 = V_L^2 / X_L \quad Q_C = V_C \cdot I_C = X_C \cdot I_C^2 = V_C^2 / X_C \quad Q = Q_L - Q_C \quad (VA_R)$$

$$S = V_T \cdot I_T = Z \cdot I_T^2 = V_T^2 / Z \quad (VA)$$

$$P = V_T \cdot I_T \cdot \cos(\phi) \quad (W) \quad Q = V_T \cdot I_T \cdot \sin(\phi) \quad (VA_R)$$

Trigonometria

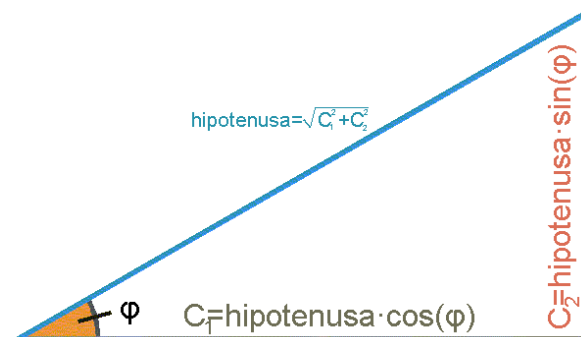

Exemple: Càlcul en 'D' Degree

$$\text{Si } \cos(\phi) = 0.8$$

Busquem l'angle

$$\cos^{-1}(0.8) = \phi = 36.87^\circ$$

Busquem el sinus

$$\sin(36.87) = 0.6$$

$$V_T = \sqrt{V_R^2 + (V_L - V_C)^2} \quad V_R = V_T \cdot \cos(\phi) \quad V_L - V_C = V_T \cdot \sin(\phi) \quad (V)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad R = Z \cdot \cos(\phi) \quad X_L - X_C = Z \cdot \sin(\phi) \quad (\Omega)$$

$$S = \sqrt{P^2 + Q^2} \quad P = S \cdot \cos(\phi) \quad Q = S \cdot \sin(\phi) \quad (VA, W, VA_R)$$

$$\phi = \arctg\left(\frac{V_L - V_C}{V_R}\right) = \arctg\left(\frac{X_L - X_C}{R}\right) = \arctg\left(\frac{Q}{P}\right) \quad (^\circ) \quad \tan \phi = \frac{Q}{P}$$

$$\text{Factor de potencia (fp)} = \cos(\phi) = \frac{P}{S} = \frac{R}{Z} \quad I = \frac{P}{V \cdot \cos \phi} \quad (A)$$

Compensació FP

$$Q_C = P \cdot (\tan \phi_1 - \tan \phi_2) \quad (VA_R) \quad C = \frac{Q_C}{2 \cdot \pi \cdot f \cdot V^2} \quad (F)$$

Corrent trifàsica

Estrella (Y)

$$V_L = \sqrt{3} \cdot V_F \quad (\text{V})$$

$$I_L = I_F \quad (\text{A})$$

Triangle (Δ)

$$V_L = V_F \quad (\text{V})$$

$$I_L = \sqrt{3} \cdot I_F \quad (\text{A})$$

Potències trifàsiques

$$P = \sqrt{3} \cdot I_L \cdot V_L \cdot \cos \varphi \quad P = 3 \cdot I_F \cdot V_F \cdot \cos \varphi \quad P = S \cdot \cos \varphi \quad (\text{W})$$

$$Q = \sqrt{3} \cdot I_L \cdot V_L \cdot \sin \varphi \quad Q = 3 \cdot I_F \cdot V_F \cdot \sin \varphi \quad Q = S \cdot \sin \varphi \quad (\text{VA}_R)$$

$$S = \sqrt{3} \cdot I_L \cdot V_L \quad S = 3 \cdot I_F \cdot V_F \quad S = \sqrt{P^2 + Q^2} \quad (\text{VA})$$

Compensació FP

$$Q_C = P \cdot (\tan \varphi_1 - \tan \varphi_2) \quad (\text{VA}_R)$$

$$C_Y = \frac{Q_C}{6 \cdot \pi \cdot f \cdot V^2} \quad (\text{F})$$

$$C_\Delta = \frac{Q_C}{2 \cdot \pi \cdot f \cdot V^2} \quad (\text{F})$$

Intensitat en trifàsic

$$I_L = \frac{P}{\sqrt{3} \cdot V_L \cdot \cos \varphi} \quad (\text{A})$$

Motor asíncron

$$n_s = \frac{60 \cdot f}{n_{pp}^\circ} \quad (\text{r.p.m.})$$

$$s = \frac{n_s - n}{n_s} \cdot 100 \quad (\%)$$

$$\eta = \frac{P_{\text{útil}}}{P_{\text{absorbida}}} \cdot 100 \quad (\%)$$

$$\omega = n \cdot \frac{2 \cdot \pi}{60} \quad \left(\frac{\text{rad}}{\text{s}}\right)$$

$$\tau = \frac{P}{\omega} \quad (\text{N} \cdot \text{m})$$